

**SECTION A : 75 MARKS**  
**BAHAGIAN A : 75 MARKAH**

**INSTRUCTION**

This section consists of **THREE (3)** structured question. Answer **ALL** questions.

**ARAHAN:**

Bahagian ini mengandungi **TIGA (3)** soalan struktur. Jawab **SEMUA** soalan.

**QUESTION 1**  
**SOALAN 1**

CLO1  
C3

- a) Calculate the total resistance  $R_T$ , based on Figure 1 from point A to B.  
*Kirakan jumlah rintangan  $R_T$ , berdasarkan kepada Rajah 1 dari titik A ke B.*

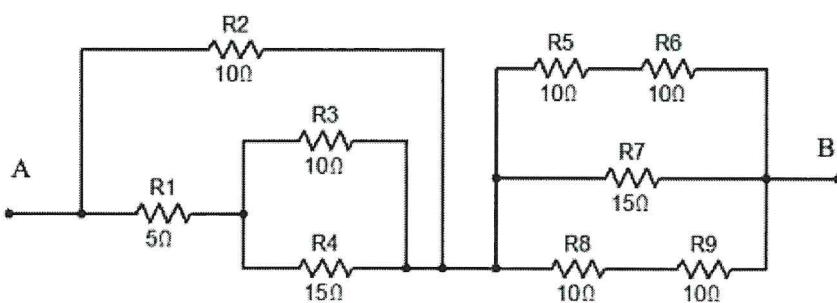


Figure 1(a)/Rajah 1(a)

[8 marks]  
[8 markah]

- b) Refer to the circuit Figure 1(b), calculate:

*Rujuk litar di Rajah 1(b), kirakan:*

- Total resistance  $R_T$   
*Jumlah rintangan  $R_T$*
- Total current  $I_T$   
*Jumlah arus  $I_T$*
- Current through  $R_2$   
*Arus melalui  $R_2$*
- Voltage drops across  $R_4$   
*Voltan susut merentasi  $R_4$*

**CLO1**  
**C3**

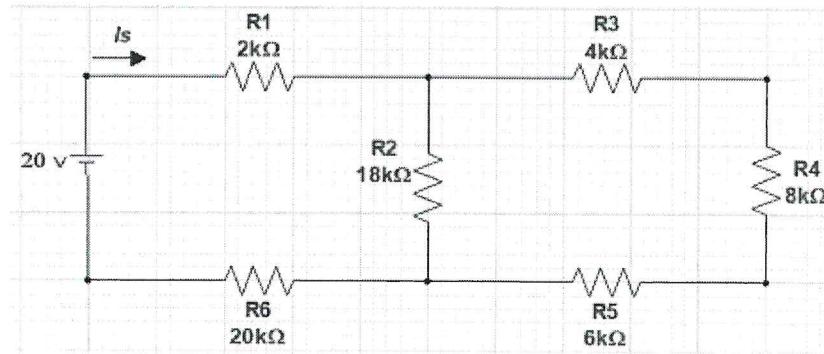


Figure 1(b)/Rajah 1(b)

[8 marks]

[8markah]

- c) Based on Figure 1(c), by using Delta – Star Transformation, calculate current flowing through resistance  $10\Omega$ .

Berdasarkan Rajah 1(c), menggunakan transformasi delta-bintang kira arus yang melalui perintang  $10\Omega$ .

**CLO1**  
**C3**

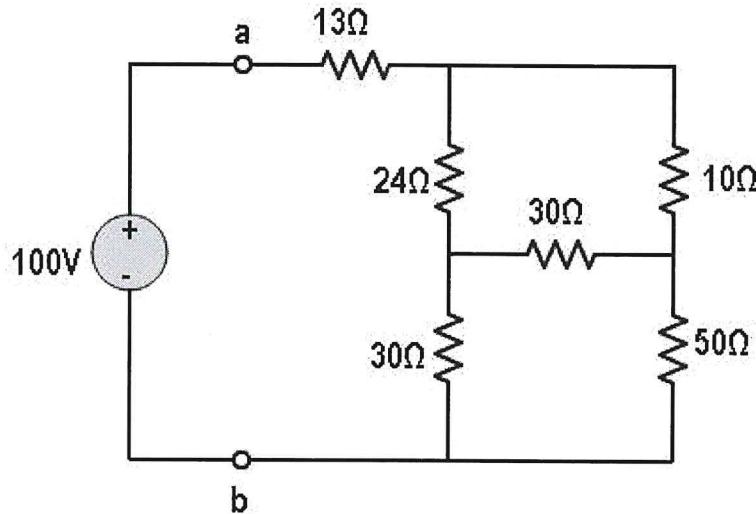


Figure 1(c)/Rajah 1 (c)

[9 marks]

[9 markah]

**QUESTION 2**  
**SOALAN 2**

CLO1  
C3

- a) By referring to the Figure 2(a) below, calculate:  
*Merujuk Rajah 2(a) di bawah, kirakan:*

i) Equivalent resistance of the circuit,  $R_{Total}$   
*Rintangan setara litar,  $R_{Total}$*

ii) Current from supply,  $I_s$   
*Arus dari bekalan,  $I_s$*

iii) Current through resistor  $R_3=150\Omega$ ,  
*Arus melalui  $R_3=150\Omega$*

iv) Voltage drop across resistor  $R_5=220\Omega$ ,  
*Voltan susut merentasi  $R_5=220\Omega$*

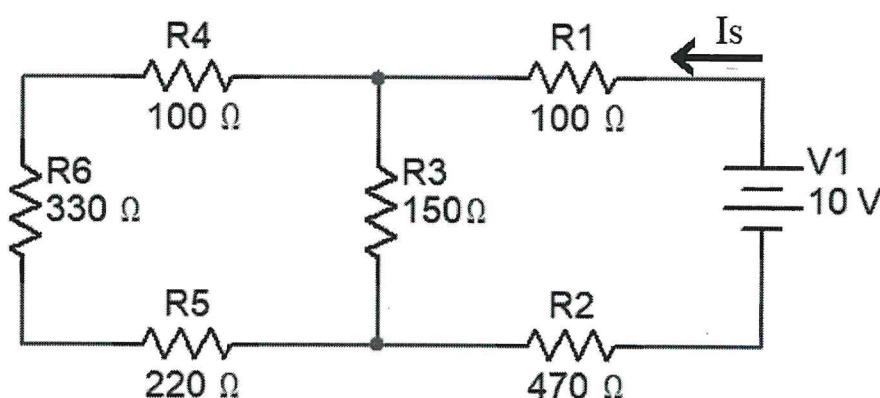


Figure 2(a) / Rajah 2(a)

[8 marks]  
[8 markah]

CLO1  
C3

- b) Calculate the total capacitance  $C_{XY}$  of the network in Figure 2(b).  
*Kira jumlah kemuatan  $C_{XY}$  bagi rangkaian dalam Rajah 2(b).*

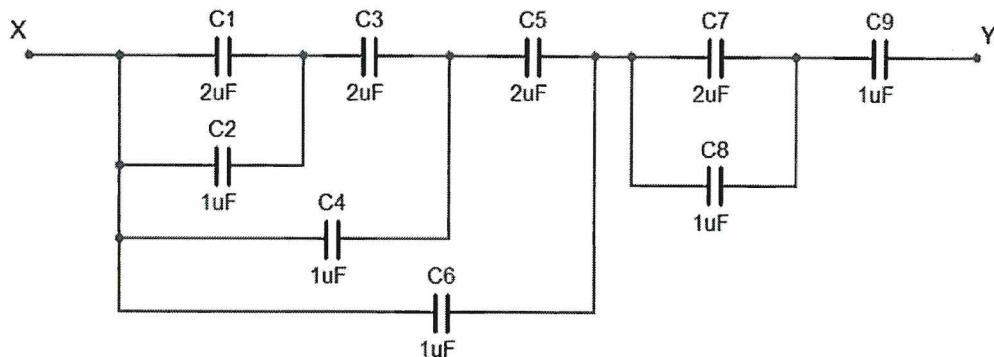


Figure 2(b) / Rajah 2(b)

[8marks]  
[8 markah]CLO1  
C3

- c) Refer to Figure 2(c), a capacitor  $100\mu F$  is charged to a voltage of  $20V$  and has a resistance of  $470 \Omega$ . Calculate:  
*Merujuk kepada Rajah 2(c), satu kapasitor  $100\mu F$  dicas pada voltan  $20V$  dan mempunyai rintangan  $470 \Omega$ . Kirakan:*

- Instantaneous value of current  $i_C$  when  $t = 47ms$   
*Nilai arus seketika,  $i_C$  apabila  $t = 47 ms$*
- Time taken to make the instantaneous value of charging voltage equals to  $10V$   
*Masa yang diambil untuk menjadikan nilai voltan pengecasan bersamaan dengan  $10V$*

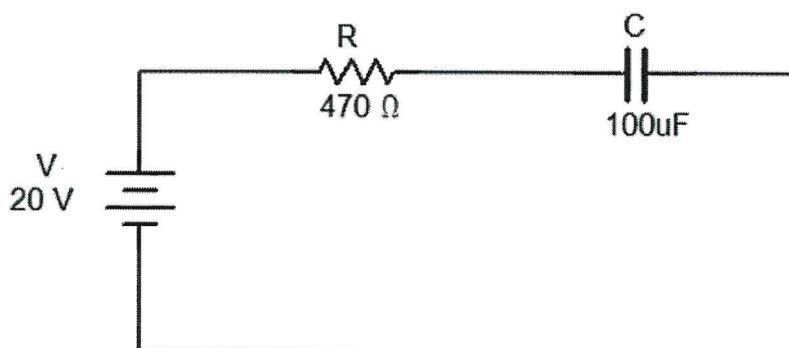


Figure 2(c) / Rajah 2(c)

[9 marks]  
[9 markah]

CLO1  
C3**QUESTION 3**  
**SOALAN 3**

- (a) Calculate the total inductance of the inductive circuit in Figure 3(a)  
*Kirakan jumlah kearuhan bagi litar inductor pada Rajah 3(a).*

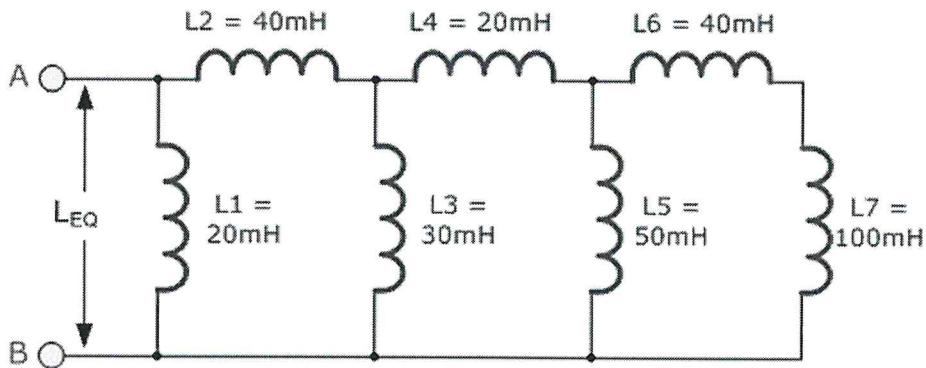


Figure 3(a)/Rajah 3(a)

[8marks]  
[8 markah]CLO1  
C3

- (b) A coil which has an inductance of  $40\text{mH}$  and a resistance of  $2\Omega$  is connected to form a LR series circuit in Figure 3 (b). If they are connected to a  $20\text{V DC}$  power supply, calculate:

*Satu gegelung mempunyai kearuhan sebanyak  $40\text{mH}$  dan rintangan  $2\Omega$  disambung pada litar siri LR pada Rajah 3(b). Jika litar ini disambung pada bekalan kuasa DC  $20\text{V}$ , kirakan :*

- Time constant,  $\tau$ .  
*Masa tetap,  $\tau$ .*
- Maximum current of inductance.  
*Arus aruhan maksima*
- Time for current rising to maximum.  
*Masa untuk arus mencapai maksima*
- Instantaneous rise current in inductor after the switch is closed for  $20\text{ms}$ .  
*Masa untuk arus seketika dalam peraruh menaik ketika suis ditutup selama  $20\text{ms}$ .*

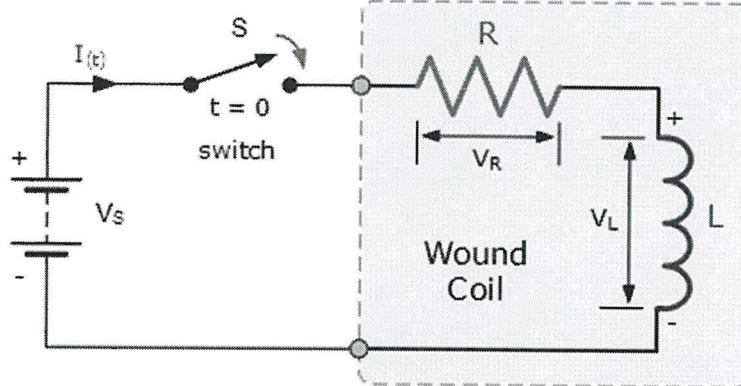


Figure 3(b)/Rajah 3(b)

[8 marks]  
[8 markah]

- (c) A coil is uniformly wound on a toroidal core. Given the value of  $\phi = 0.5\mu\text{Wb}$ ,  $N=600$  turns, cross sectional area,  $A=1 \text{ cm}^2$  and current,  $I=2\text{A}$ . Calculate magnetomotive force (m.m.f), winding flux density, the reluctance of the magnetic flux path and magnetic field strength when length,  $l = 0.3 \text{ m}$ .

CLO1  
C3

*Sebuah gegelung dibalut dengan teras toroid. Diberi nilai  $\phi = 0.5\mu\text{Wb}$ ,  $N= 600$  lilitan, luas permukaan rentas,  $A=1 \text{ cm}^2$  dan arus,  $I=2\text{A}$ . Kirakan daya gerak magnet, ketumpatan fluks lilitan, keengganan bagi laluan fluks magnet dan kekuatan medan magnet apabila panjang,  $l = 0.3 \text{ m}$ .*

[9 marks]  
[9 markah]

**SECTION B : 25 MARKS**  
**BAHAGIAN B : 25 MARKS**

**INSTRUCTION:**

This section consists of **ONE (1)** essay question. Answer **ALL** question.

**ARAHAN:**

*Bahagian ini mengandungi SATU (1) soalan esei. Jawab SEMUA soalan.*

**QUESTION 1**

**SOALAN 1**

CLO1  
C3

Based on Figure B1, calculate the value of current flow  $I_L$  through  $70\text{k}\Omega$  resistor using Thevenin and convert to Norton equivalent circuit.

*Berdasarkan Rajah B1, kirakan nilai arus  $I_L$  yang melalui perintang  $70\text{k}\Omega$  menggunakan Theorem Thevenin dan tukarkan kepada litar setara Norton.*

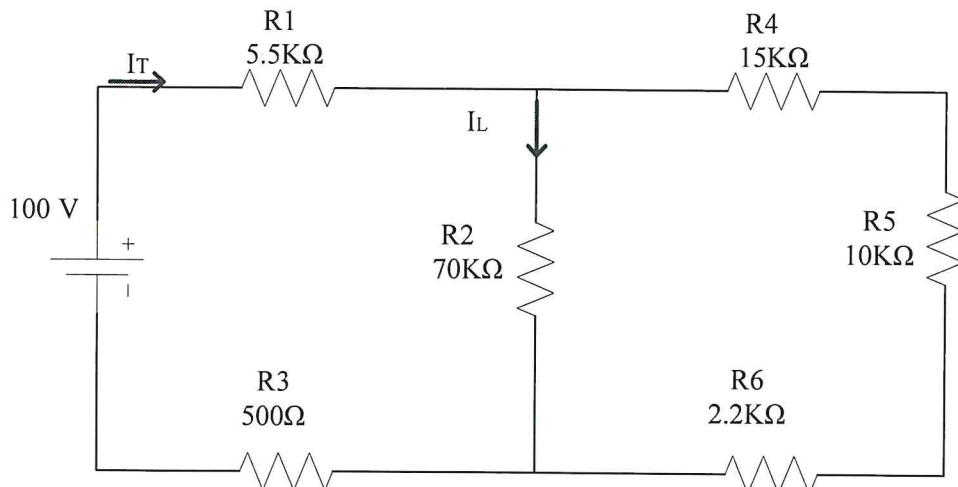


Figure B1/Rajah B1

[25 marks]  
[25 markah]

SOALAN TAMAT