

**SECTION A : 80 MARKS*****BAHAGIAN A : 80 MARKAH*****INSTRUCTION:**

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

***ARAHAN :***

*Bahagian ini mengandungi EMPAT (4) soalan berstruktur. Jawab SEMUA soalan.*

**QUESTION 1*****SOALAN 1***

- CLO1  
C1 (a) List down **FOUR (4)** types of materials that are classified within the semiconductor's family.  
*Senaraikan EMPAT (4) jenis bahan yang tergolong dalam keluarga separuh pengalir.*
- [4 marks]  
[4 markah]
- CLO1  
C2 (b) Explain the operation of forward biased voltage and the effect on the depletion layer.  
*Jelaskan operasi bagi voltan pincang hadapan dan kesannya ke atas lapisan susutan.*
- [6 marks]  
[6 markah]
- CLO1  
C3 (c) Sketch the circuit and output signal for Negative and Positive Series Clipper circuit.  
*Lakarkan litar dan isyarat keluaran untuk litar Siri Pemangkas Negatif dan Positif.*
- [10 marks]  
[10 markah]

## QUESTION 2

## SOALAN 2

CLO1  
C1

- (a) List
- FOUR (4)**
- applications of Bipolar Junction Transistor (BJT).

*Senaraikan EMPAT (4) kegunaan Bipolar Junction Transistor (BJT).*

[4 marks]

[4 markah]

CLO1  
C2

- (b) Compare the output differences of signal A, B and AB class of amplifiers.

*Bandingkan isyarat keluaran bagi kelas penguat A, B dan AB.*

[6 marks]

[6 markah]

CLO1  
C3

- (c) Based on Figure A2(c) below, calculate the value of
- $I_B$
- ,
- $I_{CQ}$
- ,
- $V_{CQ}$
- ,
- $I_{C(sat)}$
- and
- $V_{C(Cut-off)}$
- for the common emitter configuration. Given the value of
- $\beta = 60$
- and
- $V_{BE} = 0.3V$
- . (Show all calculations).

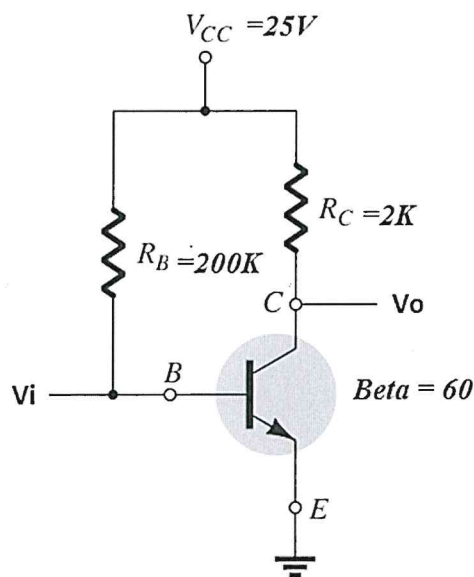
*Berdasarkan Rajah A2(c) di bawah, kira nilai bagi  $I_B$ ,  $I_{CQ}$ ,  $V_{CQ}$ ,  $I_{C(sat)}$  and  $V_{C(Cut-off)}$  untuk konfigurasi pemancar sepunya. Diberi nilai  $\beta = 60$  dan  $V_{BE} = 0.3V$ . (Tunjukkan semua pengiraan).*

Figure A2(c) / Rajah A2(c)

[10 marks]

[10 markah]

## QUESTION 3

## SOALAN 3

CLO1  
C1

- (a) The figure A3(a) is the schematic symbol for P-Channel JFET. Identify A, B, C and D.

*Rajah A3(a) adalah simbol skematik bagi saluran- P JFET. Kenalpasti A, B, C dan D.*

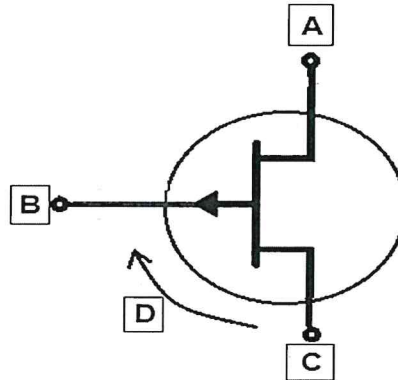


Figure A3(a) / *Rajah A3(a)*

[4 marks]  
[4 markah]

CLO1  
C2

- (b) Explain **THREE (3)** characteristics of N-channel JFET.

*Jelaskan TIGA (3) ciri-ciri N-Channel JFET.*

[6 marks]  
[6 markah]

CLO1  
C3

- (c) Draw the NMOS circuit as switch (using open and closed switch).

*Lukiskan litar NMOS sebagai suis (menggunakan suis terbuka dan tertutup).*

[10 marks]  
[10 markah]

## QUESTION 4

## SOALAN 4

CLO1  
C1

- (a) List
- FOUR (4)**
- types of other semiconductor components.

*Senaraikan EMPAT (4) jenis komponen separuh pengalir.*

[4 marks]

[4 markah]

CLO1  
C2

- (b) Figure A4(b) shows a DIAC application as a heat control circuit. Interpret how the circuit works.

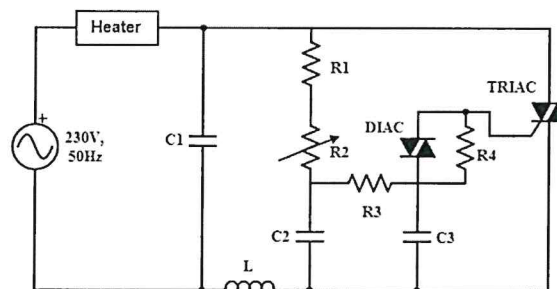
*Rajah A4(b) menunjukkan aplikasi DIAK sebagai litar pengawal suhu.**Interpretasikan bagaimana litar tersebut berfungsi.*

Figure A4 (b) / Rajah A4(b)

[8 marks]

[8 markah]

CLO1  
C2

- (c) Explain the I-V characteristics for forward and reverse bias Silicon Controlled Rectifier (SCR).

*Jelaskan ciri-ciri I-V terhadap pincang hadapan dan songsang untuk Silicon Controlled Rectifier (SCR).*

[8 marks]

[8 markah]

**SECTION B : 20 MARKS*****BAHAGIAN B : 20 MARKAH*****INSTRUCTION:**

This section consists of **ONE (1)** essay question. Answer the question.

***ARAHAN:***

*Bahagian ini mengandungi SATU (1) soalan esei. Jawab soalan tersebut.*

**QUESTION 1*****SOALAN 1***

CLO1  
C3

Sketch a center-tapped full-wave rectifier circuit with the direction of current flow. The load resistor,  $R_L$  is  $2K\Omega$  and the diode resistance is neglected. If the peak to peak voltage across the secondary winding is  $220V_{pp}$ , calculate Output Voltage ( $V_o$ ), average voltage ( $V_{avg}$ ) and average current ( $I_{avg}$ ).

*Lakarkan gambarajah litar penerus gelombang penuh sadap tengah berserta arah pengaliran arusnya. Nilai rintangan beban,  $R_L$  ialah  $2K\Omega$  dan rintangan diod diabaikan. Sekiranya bekalan voltan puncak ke puncak merentasi bahagian sekunder ialah  $220V_{pp}$ , kirakan voltan keluaran ( $V_o$ ), Voltan Purata ( $V_{avg}$ ) dan arus purata ( $I_{avg}$ ).*

[20 marks]

[20 markah]

**SOALAN TAMAT**