

**SECTION A : 80 MARKS**  
**BAHAGIAN A : 80 MARKAH**

**INSTRUCTION:**

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

**ARAHDAN:**

Bahagian ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab **SEMUA** soalan.

**QUESTION 1****SOALAN 1**

- CLO1 (a) List **TWO (2)** methods to generate an alternating current.

*Senaraikan DUA (2) kaedah untuk menjana arus ulangalik.*

[4 marks]  
[4 markah]

- CLO1 C2 (b) Explain briefly Faraday's and Lenz's Law involved in generating an alternating current.

*Terangkan dengan ringkas Hukum Faraday dan Hukum Lenz dalam menjana arus ulang alik*

[6 marks]  
[6 markah]

- CLO1 C3 (c) An alternating current voltage is given by  $v = 75 \sin(200\pi t - 0.25)$  volt.

*Calculate :*

- The peak-to-peak voltage value
- The mean voltage value
- The time period and frequency
- The value of the voltage when  $t = 8$  ms

*Satu persamaan voltan arus ulang alik adalah  $v = 75 \sin(200\pi t - 0.25)$  volt.*

*Kirakan:*

- Nilai voltan puncak ke puncak*
- Nilai voltan purata*
- Nilai tempoh masa dan frekuensi*
- Nilai voltan apabila  $t = 8$  ms*

[10 marks]  
[10 markah]

## QUESTION 2

## **SOALAN 2**

- CLO1 (a) With the aid of an appropriate diagram, explain the effects of changing frequency to RLC series circuit.

Dengan bantuan gambarajah yang sesuai, terangkan kesan perubahan frekuensi terhadap litar siri RLC.

[5 marks]  
[5 markah]

- CLO1 (b) Express the resonant frequency equation for RLC series circuits.

Terbitkan persamaan bagi frekuensi salun untuk litar siri RLC.

[5 marks]  
[5 markah]

- CLO1  
C3

(c) A coil of inductance 100mH is connected in series with a capacitance of  $2\mu\text{F}$  and a resistance of  $10\Omega$  across a 240V, variable frequency supply. Calculate the resonant frequency, the current at resonance, voltages across inductor and capacitor at resonance and Q-factor of the circuit.

Satu gegelung pearuh  $100mH$  disambungkan secara siri dengan pemuat  $2\mu F$  dan perintang  $10\Omega$  merintangi bekalan voltan  $240V$ , frekuensi boleh ubah. Kira frekuensi salun, arus ketika salun, voltan merintangi pearuh dan pemuat ketika salun dan faktor- $O$  dalam litar.

[10 marks]  
[10 markah]

**QUESTION 3*****SOALAN 3***

- CLO1      (a) List **FOUR (4)** types of transformer.  
 C1              *Senaraikan **EMPAT (4)** jenis pengubah.*

[4 marks]

[4 markah]

- CLO1      (b) Outline **SIX (6)** characteristics of an ideal transformer.  
 C2              *Kenal pasti **ENAM (6)** ciri pengubah unggul.*

[6 marks]

[6 markah]

- CLO1      (c) Referring to Figure A3 (c), calculate  $V_P$ ,  $V_S$ ,  $I_P$  and  $I_S$ .  
 C3              *Merujuk Rajah A3(c), kirakan  $V_P$ ,  $V_S$ ,  $I_P$  dan  $I_S$ .*

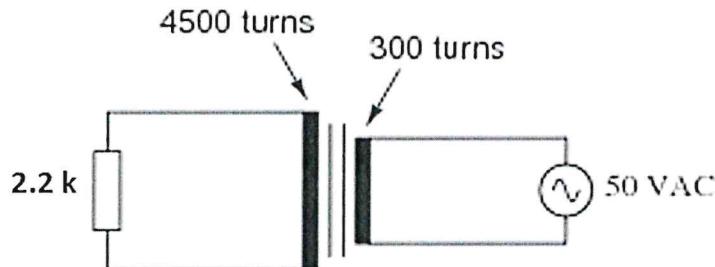


Figure A3(c) / Rajah A3

[10 marks]  
[10 markah]

**QUESTION 4****SOALAN 4**

- CLO1 (a) List **FOUR (4)** advantages of a three phase system.

*Senaraikan **EMPAT (4)** kelebihan bagi sistem tiga fasa.*

[4 marks]

[4 markah]

- CLO1 (b) With the aid of a diagram, detail the circuit diagram for three phase system in  
C2 STAR connection.

*Dengan bantuan gambarajah, perincikan rajah litar bagi sistem tiga fasa  
sambungan BINTANG.*

[6 marks]

[6 markah]

- CLO1 (c) A three-phase load are supplied with line voltage 415V and frequency 50Hz. Each  
C3 phase consists of  $15\Omega$  resistor and connected in series with inductor, 0.05H in  
DELTA connection. Calculate the phase and line current.

*Sebuah beban tiga fasa dibekalkan dengan voltan talian 415V dan frekuensi  
50Hz. Setiap fasa terdiri daripada perintang  $15\Omega$  yang disambung secara sesiri  
dengan induktor 0.05H dalam sambungan DELTA. Tentukan nilai arus fasa dan  
arus talian.*

[10 marks]

[10 markah]

**SECTION B : 20 MARKS**  
**BAHAGIAN B : 20 MARKAH****INSTRUCTION:**

This section consists of **ONE (1)** essay questions. Answer the question.

**ARAHAN:**

*Bahagian ini mengandungi SATU (1) soalan esei. Jawab soalan.*

**QUESTION 1**  
**SOALAN 1**

- CLO1  
C3 A circuit consist of a resistor connected in series with a capacitor and true power 100W at a power factor of 0.5 and voltage supply 240V, 50Hz. Calculate current flowing in the circuit, the phase angle, the resistance value, the total impedance, the capacitance value, the potential difference at each component and draw the voltage phasor diagram.

*Satu litar yang mengandungi perintang yang disambung secara siri dengan pemuat dan mempunyai kuasa sebenar 100W pada faktor kuasa 0.5 dan voltan bekalan 240V, 50Hz. Kirakan arus yang mengalir dalam litar, sudut fasa, nilai perintang, jumlah galangan, nilai kemudahan, beza upaya pada setiap komponen dan lukis gambarajah fasa bagi voltan.*

[20 marks]

[20 markah]

**SOALAN TAMAT**